

## NJM2377–Boost DC/DC Converter

Table of component models used in the Design Kit

Code	Classification	Part No.	Manufacturer	SPEC
U1	PWM-IC	NJM2377	New Japan Radio Co., Ltd.	(2.7 to 18V, 50mA)
Q1	NPN-BJT	2SD2623	Panasonic	20V / 0.5A
D1	Schottky Barrier Diode (SBD)	HRU0302A	RENESAS	20V / 0.3A

Simulation files are stored in folders, as shown in list below.

### Simulations

### Folder name

- |  |                |
|--|----------------|
| 1. NJM2377 – Soft Start Time Setting (Simulation)..... | \IC-Config\SS  |
| 2. NJM2377 – Oscillation Frequency Setting.....        | \IC-Config\OSC |
| 3. Error Amp Feed Back Loop (Transient).....           | \IC-Config\FB  |
| 4. Start-Up Transient Simulation (0~90ms.).....        | Transient      |
| 5. Efficiency and Losses.....                          | Efficiency     |
| 6. Step-Load Response.....                             | Step-load      |
| 7. Voltage and Current Simulation.....                 | Stress         |
| 8. Switching Waveforms.....                            | Waveforms      |

※ Please copy the folder named “Simulation” to your PC. Library files (.lib) are already added.

## Design document: **NJM2377–Boost DC/DC Converter**

### Contents

1. NJM2377 – Boost DC/DC Converter Circuit
2. PWM – Boost DC/DC Converter Basic Operation and Design
  - 2.1 Boost DC/DC Converter –  $V_{OUT}$
  - 2.2 Boost DC/DC Converter –  $t_{ON}/t_{OFF}$
  - 2.3 Boost DC/DC Converter – Inductor Selection
  - 2.4 Boost DC/DC Converter – Inductor Peak Current
  - 2.5 Boost DC/DC Converter –  $C_{OUT}$  Selection
3. NJM2377 – Application Circuit Configuration
  - 3.1 NJM2377 – Soft Start Time Setting
  - 3.2 NJM2377 – Oscillation Frequency Setting
  - 3.3 Error Amp Feed Back Loop Setting
4. Performance Characteristics
  - 4.1 Output Start-Up Voltage and Current
  - 4.2 Output Ripple Voltage
  - 4.3 Efficiency
  - 4.4 Step-Load Response
5. Voltage and Current Simulation Result
6. Losses
  - 6.1 Bipolar Junction Transistor Losses
  - 6.2 Schottky Barrier Diode Losses
7. Waveforms
  - 7.1 Start-Up Sequencing Waveforms
  - 7.2 Switching Waveform at Load 50mA
  - 7.3 Switching Waveform at Load 10mA

Simulations index

Simulations Settings