

DC Motor Speed Control Circuit

Table of component models used in the Design Kit

Code	Classification	Part No.	Manufacturer	SPEC
U1	IC TIMER	LM555	National Semiconductor	-
U2	DC Magnet Motor	RS-380PH	MABUCHI MOTOR	12V
U3	VOLTAGE REGULATOR	uPC7812A	NEC Electronics Corporation	12V (TYP.)
Q1	NPN-BJT	2SC1061	MOSPEC	50V / 3A
Q2	NPN-BJT	BC547	FAIRCHILD	45V / 0.1A
D1 ,D2	High-speed diodes	1N4148	PHILIPS	100V / 0.2A
D3,D4 ,D5, D6,D7	General Rectifier Diode	1N4001	EIC	50V / 1A

Simulation files are stored in folders, as shown in list below.

Simulations

Folder name

- | | |
|---|-------------------------------------|
| 1. Transient Response at No Load (Model)..... | \Simulations\Transient\Trans_NoLoad |
| 2. Speed at No Load (Model)..... | \Simulations\Transient\Speed_NoLoad |
| 3. The Motor Steady-State Current Condition Setting (1/2).. | \Simulations\Transient\Steady State |
| 4. The Motor Steady-State Current Condition Setting (2/2).. | \Simulations\Transient\Trans_1A1 |
| 5. Transient Response at Load 3.8A..... | \Simulations\Transient\Trans_3A8 |
| 6. LM555 DC Motor Speed Control Circuit (No Load)..... | \Simulations\Trans_NoLoad |
| 7. LM555 DC Motor Speed Control Circuit (Fan Load)..... | \Simulations\Trans_FanLoad |

※ Please copy the folder named “Simulations” to your PC. Library files (.lib) are added already.

Design document: **DC Motor Speed Control Circuit**

Contents

- 1. The Simulation of DC Motor Control Circuit.....
- 2. DC Motor Model
 - 2.1 Manufacturer Specification.....
 - 2.2 Torque Constant and Back EMF Constant.....
 - 2.3 The Armature Inductance and Resistance.....
 - 2.4 The DC Motor Equivalent Circuit.....
 - 2.5 Transient Response at No Load.....
 - 2.6 Transient Response at No Load (Model).....
 - 2.7 Speed at No Load (Model).....
 - 2.8 The Motor Steady-State Current Condition Setting.....
 - 2.9 Transient Response at Load 3.8A (Measurement vs. Simulation).....
- 3. LM555 DC Motor Speed Control Circuit (No Load).....
 - 3.1 Rectified dc voltage with ripple.....
 - 3.2 IC 555 Output Pulse Voltage.....
 - 3.3 Transistor Q2: VCE.....
 - 3.4 Transistor Q1: VCE, IC.....
 - 3.5 Motor Voltage and Current.....
- 4. LM555 DC Motor Speed Control Circuit (Fan Load).....
 - 4.1 Rectified dc voltage with ripple.....
 - 4.2 IC 555 Output Pulse Voltage.....
 - 4.3 Transistor Q2: VCE.....
 - 4.4 Transistor Q1: VCE, IC.....
 - 4.5 Motor Voltage and Current.....

Simulations index

Simulation Settings